

CONTENTS IN DETAIL

ACKNOWLEDGMENTS	XIII
INTRODUCTION.....	2
THE CIRCUITS	2
THE MATERIALS.....	3
HOW TO BUILD THE CIRCUITS IN THIS BOOK	5
WHAT THE COMPONENTS LOOK LIKE.....	5
BUILDING CIRCUITS ON A BREADBOARD	8
BUILD YOUR FIRST BREADBOARD CIRCUIT	10
THE CIRCUIT DIAGRAM	11
THE PARTS LIST.....	11
BUILDING THE CIRCUIT.....	11
CONNECTING THE RESISTOR	11
CONNECTING THE LED	12
CONNECTING TO THE POWER SUPPLY COLUMNS.....	13
CONNECTING THE BATTERY.....	14
WHAT IF THE LED DOES NOT LIGHT UP?	15
YOU'RE READY TO BUILD THE NINE CIRCUITS!	15
PROJECT 1: THE STEADY-HAND GAME.....	16
THE CIRCUIT DIAGRAM	17
THE PARTS LIST.....	17
ABOUT THE CIRCUIT.....	17
CONNECTING THE BATTERY TO THE BUZZER.....	18
CREATING THE GAME TRACK	18
CONNECTING THE METAL RING TO THE BREADBOARD	19
COMMON MISTAKES	20
A QUIET ALTERNATIVE	20
PROJECT 2: THE TOUCH-ENABLED LIGHT	21
THE CIRCUIT DIAGRAM	22
THE PARTS LIST.....	22
INTRODUCING THE TRANSISTOR	22
ABOUT THE CIRCUIT.....	23
COMMON MISTAKES	24
HOW THE CIRCUIT WORKS.....	24

PROJECT 3: THE COOKIE JAR ALARM	26
THE CIRCUIT DIAGRAM	27
THE PARTS LIST.....	27
ABOUT THE CIRCUIT.....	27
COMMON MISTAKES	28
HOW THE CIRCUIT WORKS.....	28
PROJECT 4: THE NIGHT-LIGHT	30
THE CIRCUIT DIAGRAM	31
THE PARTS LIST.....	31
ABOUT THE CIRCUIT.....	31
COMMON MISTAKES	32
HOW THE CIRCUIT WORKS.....	32
PROJECT 5: THE BLINKING LED	35
THE CIRCUIT DIAGRAM	36
THE PARTS LIST.....	36
ABOUT THE CIRCUIT.....	36
COMMON MISTAKES	38
HOW THE CIRCUIT WORKS.....	39
PROJECT 6: THE RAILROAD CROSSING LIGHT.....	42
THE CIRCUIT DIAGRAM	43
THE PARTS LIST.....	43
ABOUT THE CIRCUIT.....	43
COMMON MISTAKES	43
HOW THE CIRCUIT WORKS.....	44
PROJECT 7: THE PARTY LIGHTS	48
THE CIRCUIT DIAGRAM	49
THE PARTS LIST.....	49
ABOUT THE CIRCUIT.....	49
COMMON MISTAKES	50
HOW THE CIRCUIT WORKS.....	50
PROJECT 8: THE DIGITAL PIANO.....	54
THE CIRCUIT DIAGRAM	55
THE PARTS LIST.....	55
ABOUT THE CIRCUIT.....	55
COMMON MISTAKES	57
HOW THE CIRCUIT WORKS.....	57

PROJECT 9: THE LED MARQUEE	59
THE CIRCUIT DIAGRAM	60
THE PARTS LIST.....	60
ABOUT THE CIRCUIT.....	60
COMMON MISTAKES	61
HOW THIS CIRCUIT WORKS	62
WHERE TO GO FROM HERE	63
RESISTOR COLOR CODES	64